

## Question

Please analysis this force sensing application and design the amplifier gain and the the gain register( $R_G$ ) of the instrumentation amplifier as shown in below Figure 1 (where  $R_1=R_2=25\text{ K}\Omega$ )

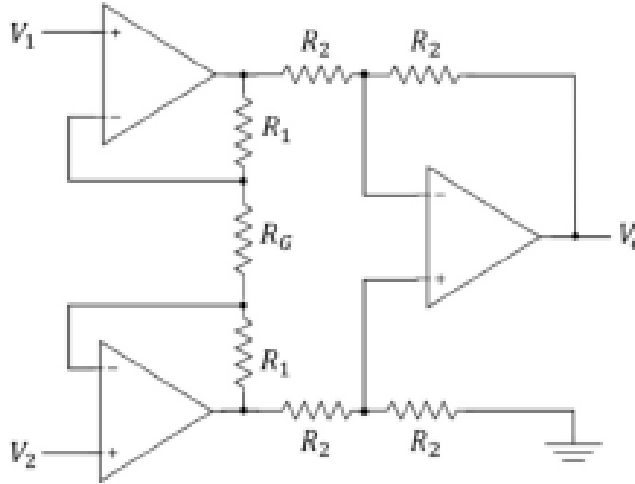


Figure 1: ADC structure

## Analysing

Firstly, we know that the force sensor is used to measure a contact force which range is from 0 to 2 N. After seeing the key metric of this force sensor specifications, the sensitivity(60 mv/N) of this force sensor is crucial to calculate the output range of force sensor. Here are the results:

$$V_{force} = 60 * 2 = 120mv = 0.12V \quad (1)$$

Then, we focus on the ADC(Analog-to-digital converter) part. At the same time, we know that the requirement of output of this ADC is range from -10V to 10 V, so we can get the output range of ADC.

$$V_{ADC} = 10 - (-10) = 20v \quad (2)$$

Based on the requirement of this question, we should know that the amplifier gain in Figure 2 is at least  $\frac{V_{ADC}}{V_{force}}$ .

$$A_V = \frac{V_{ADC}}{V_{force}} \approx 167 \quad (3)$$


Following the definition of Amplifier gain in lecture notes, we can use the calculation equation of amplifier to get the result of  $R_{gain}$

$$A_V = \frac{V_{ADC}}{V_{force}} = \left(1 + \frac{2R_1}{R_{gain}}\right) \frac{R_3}{R_2} \quad (4)$$
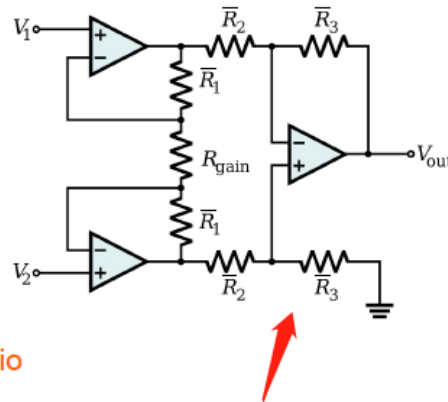
## Force Sensors

- **Instrumentation Amplifier**

- A special type of *differential amplifier*
- **Features**
  - Very low DC offset
  - Low drift
  - Low noise
  - Very high open-loop gain
  - Very high common-mode rejection ratio
  - Very high input impedances
- **Amplifier Gain**
  - Adjust by only one resistor



**R2=R3**

$$A_v = \frac{V_{out}}{V_2 - V_1} = \left(1 + \frac{2\bar{R}_1}{R_{gain}}\right) \frac{\bar{R}_3}{\bar{R}_2}$$

Figure 2: Definitions in the lecture notes

Finally, through the specification of this ADC( $R_2 = R_3$ ), as a result, we can get the  $R_{gain}$  from this below equation.

$$R_{gain} = \frac{2R_1}{A_v - 1} \approx 301\Omega \quad (5)$$

## Conclusions

### Force sensing application

This force sensing application: The system use the force sensor to sense the range of force, and then amplify this signal by using this amplifier. As a result, ADC get the correct signal from a special filter. In a word, through this process in Figure 3 and calculating transformation, the user can know the variety of the initial force.

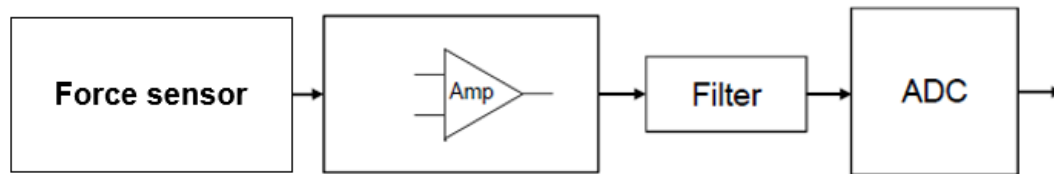


Figure 3: The total process of force sensing application

### Amplifier gain

From the result in Analysing part, the Amplifier gain is about 167.

### Gain resistor

Through the calculation in Analysing part, the gain resistor is about  $301\Omega$ .